

H8/300L

Driving of Stepper Motor (Stepper)

Introduction

A stepper motor translates current pulses into motor rotation. A typical stepper motor contains 4 winding coils. Applying voltage to these coils forces the motor to rotate step by step.

In normal operation, two winding coils are activated at the same time. The stepper motor moves clockwise one step per change in winding activated. If the sequence is applied in reverse order, the motor will run counterclockwise.

The speed of rotation is controlled by the frequency of the pulses. Every time a pulse is applied to the stepper motor the motor will rotate a fixed distance. A typical step rotation is 18 degrees. With 18 degrees rotation in each step will complete one rotation of the motor (360 degrees) require 20 steps. By changing the interval time, the speed of the motor can be regulated, and by counting the number of steps, the rotation angle can be controlled.

I/O port 5 [bit 3 ..bit 0] of H8/38024 MCU is used to drive the 2 phase / 4 phase stepper motor driver circuit. Two types stepper motor driver circuit will be introduce here, first is stepper motor driver IC (L298N) and second is power MOSFET transistor (2SK1095).

This application note demonstrated the use of H8/38024F SLP MCU in driving a 2 phase / 4 phase stepper motor. Two types of hardware driver circuits are discussed.

Target Device

H8/300L Super Low Power – H8/38024 Series

Contents

1. HARDWARE OVERVIEW.....	3
1.1 Hardware Circuit Option 1:.....	3
1.2 Hardware Circuit Option 2:.....	7
2. Software Overview.....	9
2.1 Software description for Example source code 1	9
2.2 Software description for example source code with timer interrupt.....	14
3. Other Consideration.....	14
Reference.....	14

1. HARDWARE OVERVIEW

 


Figure 1 Hardware Block Diagram

Basically, there are 3 components in the stepper motor control circuit:

- Micro-controller - used to generate the stepper motor control waveforms
- Motor Driver - used to drive the stepper motor
- Stepper Motor - used to evaluate the control waveform from MCU

1.1 Hardware Circuit Option 1:

In hardware design, the most complicated part is stepper motor driver circuit design. This motor driver design depends on the stepper motor characteristic. The most common way to design a stepper motor driver is using a “Stepper Motor Driver IC”. The stepper motor that I choose is SAIA-UAG2 which can connect 2-phase or 4-phase. Table 1 and table 2 show the technical data of two different stepper motor which can be used in this application note.

The L298N stepper motor driver circuit diagram (2-phase) is show by figure 2 and the R1 and R2 value depend from the load current. The protection diodes also can be reduce by changing the IC L298N to L293D.

Table 1 Technical data of SAIA-UAG2 stepper motor:

Item	Value		
Step per resolution	20		
Winding type	Unipolar		
Rated Voltage	6 volt	12 volt	24 volt
Resistance per winding	35 Ω	170 Ω	700 Ω
Maximum Power Consumption	0.4 Watt		
Winding temperature	130°C		
Duty Cycle	100%		
Holding torque	0.5 cNm		
Detent torque	0.14 cNm		
Direction of rotation	Reversible		
Rotor inertia	0.31 gcm ²		



Table 2 Technical data of Step-Syn (type:103H546-0440) stepping motor:

Item	Value
Step per resolution	200
Rated Voltage	3.15 volt
Resistance per winding	3.15 Ω
Current per phase	1 Ampere
Holding torque	1.5 kg.cm
Direction of rotation	Reversible
Rotor inertia	31 gcm ²
Weight	0.2 kg



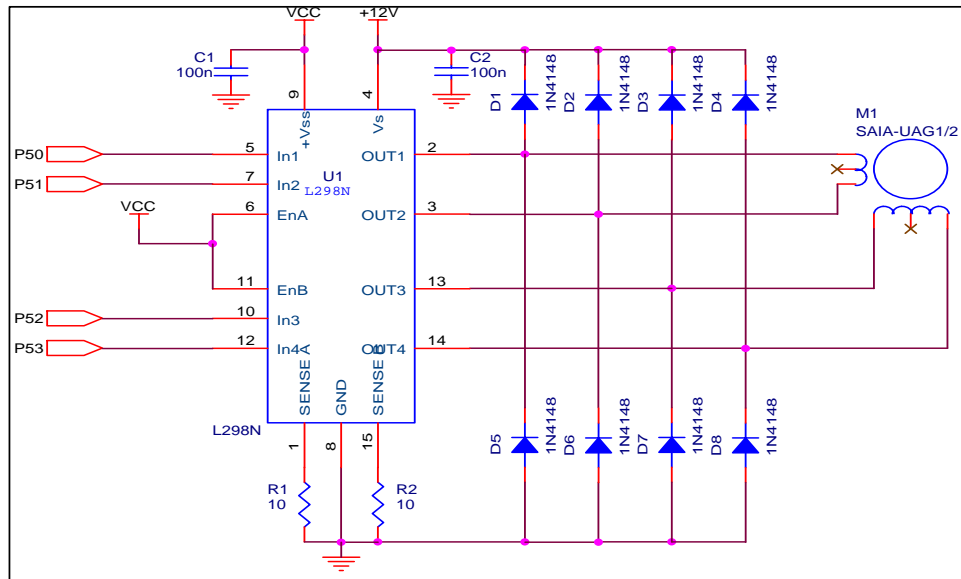


Figure 2 L298N Stepper Motor Driver Circuit(2-phase)

Table 3: Full-step sequencing

Step	P53	P52	P51	P50	PDR5
0	1	0	0	1	0x09
1	1	0	1	0	0x0A
2	0	1	1	0	0x06
3	0	1	0	1	0x05

Table 4: Half-step sequencing

Step	P53	P52	P51	P50	PDR5
0	1	0	0	0	0x08
1	1	0	1	0	0x0A
2	0	0	1	0	0x02
3	0	1	1	0	0x06
4	0	1	0	0	0x04
5	0	1	0	1	0x05
6	0	0	0	1	0x01
7	1	0	0	1	0x09

 


Figure 3 Waveform for Hardware circuit option 1 with example program 1

1.2 Hardware Circuit Option 2:

Besides using the stepper motor driver IC, stepper motor can be drive by 4 N-channel MOSFET 2SK1095. Figure 4 shown the MOSFET stepper motor driver circuit(4-phase). The stepper motor control waveform are driven through AND gates.

The signals are input to the gates of 4 N-Ch. MOSFET transistors (type 2SK1095), alternately switching them on and off. These transistors act as a drain for the current generated across the stepper motor coils. Four protection diodes (type HRP-22) are used to keep the voltage drop between the drain and the source to 0.55V. Motor make a lot of electrical noise so C1 and C2 is used to suppress the noise spikes.

Finally, power is supplied to the motor windings from a +12V* power supply through a pair of resistor to limit the coils current. Since the MOSFET's switching time is extremely fast, therefore a dead-time is needed between inverting phase signals (A and A-, B and B-) so that A- and B- signal will be slightly reduce before A and B are turned on. User can also increase the dead-time delay to achieve Half-step sequent. Note that R6, R7, R8 and R9 are pulled down, if MCU is trigger to standby mode, I/O port is in high impedance thus all phase will be in inactive mode.

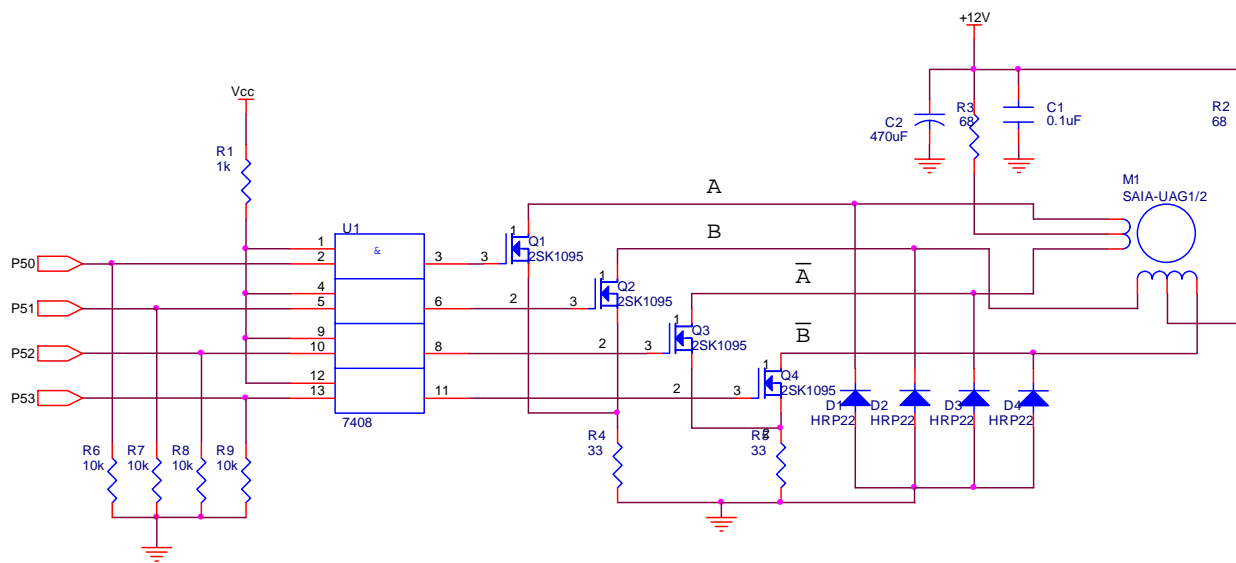


Figure 4 MOSFET Stepper Motor Driver Circuit

* User may change the +12V supply and R2, R3, R4, R5 value to suit different stepper motor. For example: Power supply = 3 volt, R2=R3=R4=R5=1Ω when use *Step-syn* stepper motor to achieve rated holding torque.

Table 5: Full-step sequencing

Step	P53	P52	P51	P50	PDR5
0	1	0	0	1	0x09
1	1	0	1	0	0x0A
2	0	1	1	0	0x06
3	0	1	0	1	0x05

Table 6: Dead-time sequencing

Step	P53	P52	P51	P50	PDR5
0	0	0	0	1	0x01
1	1	0	0	0	0x08
2	0	1	0	0	0x02
3	0	0	1	0	0x04

 


Figure 5 Waveform for Hardware circuit option 2 with example program 2

2. Software Overview

Once the desired port pins on the MCU are connected to the input pins on the stepper motor driver IC, the stepping sequence is easily implemented into software. Any I/O port on the MCU can be used to provide the input signal to the driver IC. In this example, the lower 4 bit of Port 5 is connected to the input pin of the driver IC (Hardware Circuit Option 1). To energize a winding the programmer set the “In1” pin high (binary 1) and the “In2” pin low (binary 0). The following code in figure 6 gives an example on how programmer can cause the stepper motor to continuously rotate, using the Full Stepping sequence as described in Table 3.

```
#include "iodefine.h"
#include <machine.h>

unsigned int loop_count, delay, max_step;
//an array of the positions used in the Full Stepping sequence
unsigned char motor_data[4] = {0x09,0x0a,0x06,0x05};
void main(void)
{
    P_IO.PCR5.BYTE = 0xFF; //set port 5 as output port
    P_IO.PDR5.BYTE = 0x00; //set port 5 data as 0000 0000
    loop_count = 0; max_step = 4; //Initialises the variable

    while(1)
    {
        //output stepping sequence
        P_IO.PDR5.BYTE = motor_data[loop_count++];
        //Coil energizing time
        for (delay=0 ; delay<0x300; delay++) ;
        //return to beginning
        if (loop_count==max_step) loop_count = 0;
    }
}
```

Figure 6 Example source code 1 for stepper motor control

2.1 Software description for Example source code 1

To use a different stepping sequence, simply change the motor_data and max_step value, e.g. for the Half stepping sequence, max_steps should be changed to 8 and motor_data[4] change to motor_data[8]={0x08, 0x0a, ...,0x01,0x09}; (follow the Table 5).

As the MCU executes each command within microseconds, a delay need to be inserted in between each step, otherwise the rotor will not be able to rotate as the winding is not fully energise. This has been implemented with the line

for (delay=0 ; delay<0x300; delay++) ;

where the value of delay affects the speed and torque of the motor. If the value of delay were increased, it would cause the winding to be energised for longer which would increase the torque, but because the winding is being energised for longer the speed of the motor is reduced. If the value of delay is decreased, the speed of the motor is increased however this causes the torque to be reduced and the motor may not be able to rotate or be in control.

Thus, for Hardware circuit option 2, a dead-time sequence needs to be inserted before each stepping sequence. The example source code (shown in Figure 6) has to be modified to suit the hardware circuit option 2. The following source code in Figure 7 shows the modification of the stepper motor control source code.

```
#include "iodefine.h"
#include <machine.h>

unsigned int loop_count, delay, max_step;
//an array of the positions used in the Full Stepping sequence
unsigned char motor_data[8] = {0x01, //Dead-time sequence 0
                               0x09, //stepping sequence 0
                               0x08, //Dead-time sequence 1
                               0x0A, //stepping sequence 1
                               0x02, //Dead-time sequence 2
                               0x06, //stepping sequence 2
                               0x04, //Dead-time sequence 3
                               0x05 //stepping sequence 3
                              };

void main(void)
{
    P_IO.PCR5.BYTE = 0xFF; //set port 5 as output port
    P_IO.PDR5.BYTE = 0x00; //set port 5 data as 0000 0000
    loop_count = 0; max_step = 8; //Initialises the variable
    while(1)
    {
        P_IO.PDR5.BYTE = motor_data[loop_count++]; //output deadtime sequence
        for (delay=0 ; delay<0x10; delay++) ; //small delay
        P_IO.PDR5.BYTE = motor_data[loop_count++]; //output stepping sequence
        for (delay=0 ; delay<0x300; delay++) ; //Coil energizing time
        if (loop_count==max_step) loop_count = 0;
        //return to beginning
    }
}
```

Figure 7 Example source code 2 for stepper motor control

The example source code 1 and 2 above demonstrates a simple method of implementing the stepper motor control. A more efficient method to reduce the MCU load, would be to make use of the “Timer Interrupt” to generate the stepper motor control stepping sequence. Let’s modify the example source code 2 to become a timer interrupt driven method. In this example, Timer F is chosen to generate the stepper motor control waveform.

There are 2 parts of programming when timer interrupt is used:

- a. Main program - void main(void)
- b. Interrupt service routine - __interrupt(vect=15) void INT_TimerFH(void)

*Please refer to figure 8 and figure 9 for the detail source code.

```

#include "iodefine.h"
#include <machine.h>
void init_stepper_motor_io(void);
void init_timer_F(void);

unsigned int loop_count, delay, max_step;
//an array of the positions used in the Full Stepping sequence
unsigned char motor_data[8] = {0x01, //Dead-time sequence 0
                               0x09, //stepping sequence 0
                               0x08, //Dead-time sequence 1
                               0x0A, //stepping sequence 1
                               0x02, //Dead-time sequence 2
                               0x06, //stepping sequence 2
                               0x04, //Dead-time sequence 3
                               0x05 //stepping sequence 3
                              };

void main(void)
{
    init_stepper_motor_io(); //initialise I/O port
    init_timer_F();         //initialise Timer F with interrupt
    while(1)
    {
        //user program start here
    }
}

void init_stepper_motor_io(void)
{
    P_IO.PCR5.BYTE = 0xFF;
    //set port 5 as output port

    P_IO.PDR5.BYTE = 0x00;
    //set port 5 data as 0000 0000
}

```

```
void init_timer_F(void)
{
    set_imask_ccr(1);          //disable interrupt request
    P_TMRF.TCRF.BYTE = 0x04;   //set timer F 16bit mode, counting on TCFL
                               //overflow signal
    P_TMRF.TCSRFBIT.CCLRHR = 1; //TCF clearing by compare match

    P_TMRF.OCRFBYTE.H = 0x00;
    P_TMRF.OCRFBYTE.L = 0x30;  //set output compare register value

    P_SYSCR.IENR2.BIT.IENTFH = 1; //Enable Timer F interrupt
    P_SYSCR.IRR2.BIT.IRRTFH = 0;  //clear Timer F interrupt request flag
    set_imask_ccr(0);           //enable interrupt request
}
```

Figure 8 Main program for stepper motor control (with timer interrupt)

```
#include "iodefine.h"
#include <machine.h>
extern unsigned char motor_data[8];
extern unsigned char loop_count;
#pragma section IntPRG
// vector 1 Reserved

// vector 2 Reserved

// vector 3 Reserved

// vector 4 IRQ0
__interrupt(vect=4) void INT_IRQ0(void) { /* sleep(); */ }
.
.
.
.

__interrupt(vect=14) void INT_TimerFL(void) { /* sleep(); */}
// vector 15 Timer FH Overflow
__interrupt(vect=15) void INT_TimerFH(void)
{
    if (P_TMRF.TCSRFBIT.CMFH == 1)
    {
        P_TMRF.TCSRFBIT.CMFH = 0;
        if (loop_count%2 == 0) //DEAD-TIME_DATA
        {
            P_IO.PDR5.BYTE = motor_data[loop_count++];
            P_TMRF.OCRFBYTE.H = 0x00;
            P_TMRF.OCRFBYTE.L = 0x30;
        }
    }
    else
```

```
    {
        P_IO.PDR5.BYTE = motor_data[loop_count++];
        P_TMRF.OCRFB.BYTE.H = 0x03;
        P_TMRF.OCRFB.BYTE.L = 0x00;
    }

    if (loop_count==8) loop_count = 0;
}

P_SYSCR.IRR2.BIT.IRRTFH= 0;
}
// vector 16 Timer G Overflow
__interrupt(vect=16) void INT_TimerG(void) { /* sleep(); */}
// vector 17 Reserved
```

Figure 9 Interrupt program for stepper motor control (with timer interrupt)

2.2 Software description for example source code with timer interrupt

First, the MCU will initialize the stepper motor I/O port as output port with value 0x00. Then Timer F is initialized as 16-bit free-running counter with timer clock is set to $\varnothing/32$. The Timer F counter value (TCF) will clear to 0x0000 when a compare-match between OCRF and TCF occur. Finally the timer F interrupt is enable to allow the output compare-match interrupt request from Timer F.

The process start by loading the startup count into the OCRF during the timer initialization code and Timer F interrupt service routine will do the rest of the job. The Interrupt routine is serviced when the contents of OCRF match the contents TCF. Then, the dead-time sequence data is output to Port 5, the OCRF is update for dead-time duration. After that, when OCRF match with TCF again, the second time timer interrupt request occur, this time the stepper motor sequence data is output to port 5 and OCRF is update again for dead-time duration.

Interrupt routine work as below:

- a. When timer F interrupt request occur, the interrupt service routine will be executed.
- b. Then check for compare-match flag for '1' if yes continue the rest of the process
- c. Clear CMFH flag
- d. Check for loop_count value, if EVEN number then output dead-time sequence data and then setup OCRF value for dead-time duration.
- e. If the loop_count value is ODD then stepping data will output to port 5 and update the OCRF for coil energised duration.
- f. Reset the loop_count when all the 8 sequence data was output to port 5.
- g. Clear interrupt request flag to '0'.

3. Other Consideration

The driving of stepper motor can be further enhancement, depending on the need of the application. For example, the application may need to drive the stepper motor to make numerous turns in a quickest possible time. In order to kick-start the motor, the initial delay may be longer as higher torque is required to turn the motor load. This delay can be slowly reduced due to the motor rotating inertia. In this manner, motor can be rotate in a faster speed. These delay data can be calculate based on the motor profile, load and etc.

The stepper motor used in this AN is a general low power stepper motor (400mW max), user may need to changes the driver circuit to suit the higher power stepper motor.

Reference

1. H8/38024 Series, H8/38024F-ZTAT Hardware Manual (ADE-602-231A)
2. H8/300 Using a H8/300 to control a stepper motor Application Note (AE-0057)

Revision Record

Rev.	Date	Description	
		Page	Summary
1.00	Sep.03	-	First edition issued

Keep safety first in your circuit designs!

1. Renesas Technology Corporation puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of nonflammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

1. These materials are intended as a reference to assist our customers in the selection of the Renesas Technology Corporation product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Renesas Technology Corporation or a third party.
2. Renesas Technology Corporation assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
3. All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Renesas Technology Corporation without notice due to product improvements or other reasons. It is therefore recommended that customers contact Renesas Technology Corporation or an authorized Renesas Technology Corporation product distributor for the latest product information before purchasing a product listed herein.
The information described here may contain technical inaccuracies or typographical errors. Renesas Technology Corporation assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors.
Please also pay attention to information published by Renesas Technology Corporation by various means, including the Renesas Technology Corporation Semiconductor home page (<http://www.renesas.com>).
4. When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Renesas Technology Corporation assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
5. Renesas Technology Corporation semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Renesas Technology Corporation or an authorized Renesas Technology Corporation product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
6. The prior written approval of Renesas Technology Corporation is necessary to reprint or reproduce in whole or in part these materials.
7. If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.
Any diversion or reexport contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
8. Please contact Renesas Technology Corporation for further details on these materials or the products contained therein.